

Digital Logic Design (DLD)

(Lab Task No 3)



Session (2022-2026)

Program

BS-Computer Science

Submitted By:

Student Name: Shaheer Ali

Roll Number: 301-221044

Supervised By:

Ms. Muneeba Darwaish

Lecturer

CS& IT Department

Hazara University, Mansehra

EXPERIMENT 03

Implementation of Basic Gates using Universal Gates

Objectives:

Using two input NAND and NOR gates, construct the following

1. NOT
2. AND
3. OR

After doing this, implement the given expression on the trainer board.

Equipment /Tool:


Trainer, IC 74LS00, 74LS02.

Theory:

NAND and NOR gates are called universal gates because we can make any basic gate from them by using the following circuits.

1) Implementation of Gates using NAND Gate only: i)


NOT Gate Behavior:

 

Truth Table With Proof:

Input	output	Proof
0	1	
1	0	


ii) **AND Gate Behavior:**

 

Truth Table With Proof:

Input		Output	Proof
A	B	Q	
0	0	0	
0	1	0	
1	0	0	
1	1	1	

iii) **OR Gate Behavior:**

 

2-input OR Gate


Truth Table With Proof:

Input		Output	Proof
X	Y	F	
0	0	0	
0	1	1	
1	0	1	
1	1	1	

2) Implementation of Gates using NOR Gate Only:

Verify all the truth tables for all the gates.


i) NOT Gate Behavior:

 

Truth Table With Proof:

A	A'	Proof
0	1	
1	0	


ii) AND Gate Behavior:

 

Truth Table With Proof:

A	B	Q	Proof
0	0	0	
0	1	0	
1	0	0	
1	1	1	

iii) **OR Gate Behavior:**

 

Truth Table With Proof:

A	B	F	Proof
0	0	0	
0	0	1	
1	0	1	
1	1	1	

Exercise in Lab:


- 1) Implement following expression using NOR Gate only.
- 2) Implement following expression using NAND Gate only.

$$F = X + \overline{Y} \cdot Z$$


Make Circuit Diagram By Implementing Both Methods :

Answer:

**Implementation
Using NOR
Gate Only:**

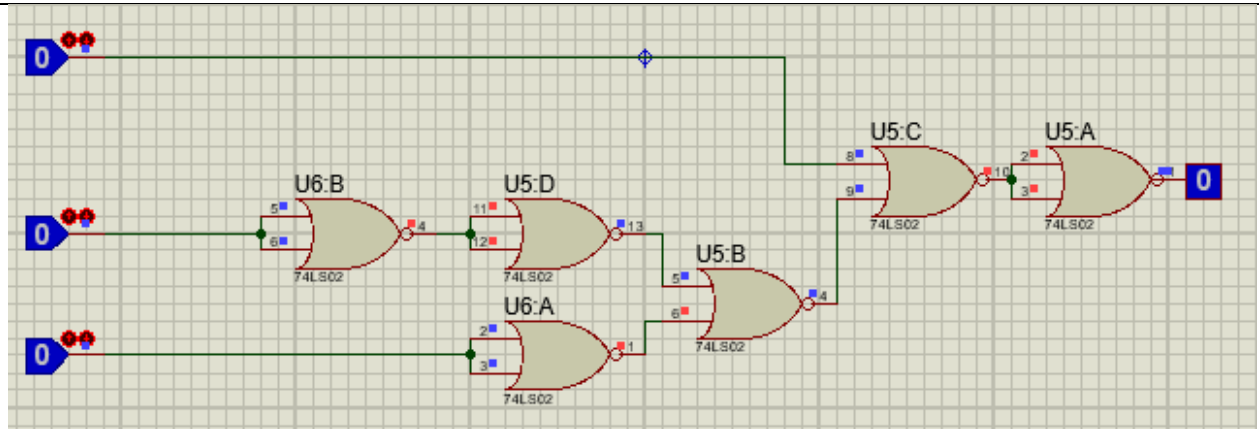





**Implementation
Using NAND
Gate Only:**

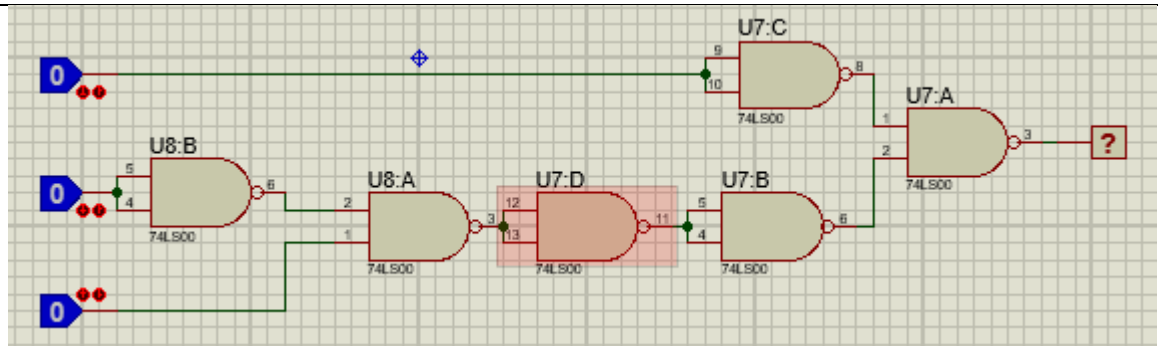

1) Implement following expression using NOR Gate only:

Answer:






Truth Table With Proof:

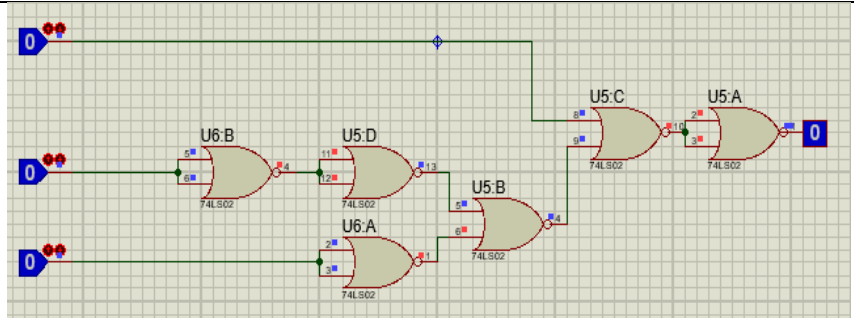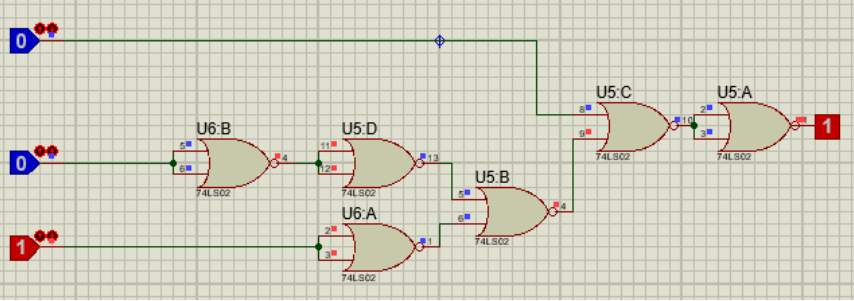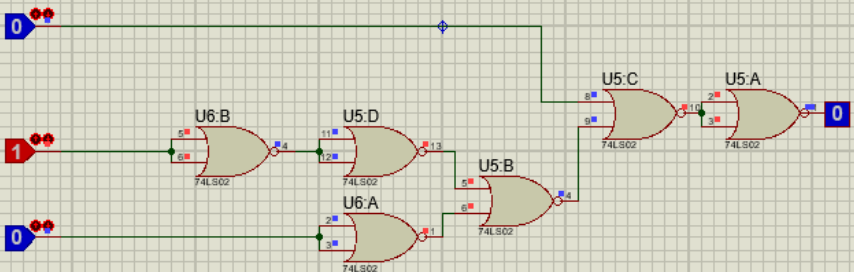
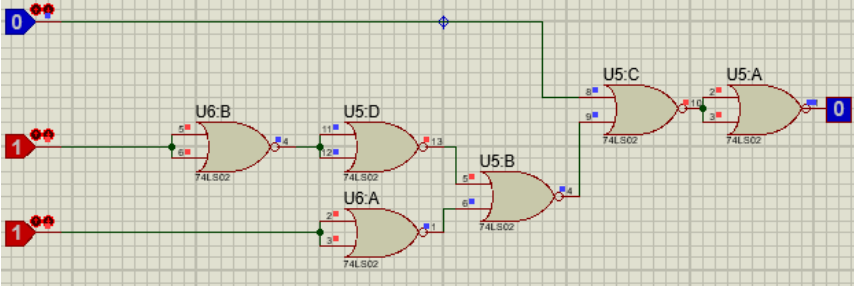
Input			Output	Proof
X	Y	Z	F	
0	0	0	0	
0	0	1	1	
0	1	0	0	
0	1	1	0	

1	0	0	1	
1	0	1	1	
1	1	0	1	
1	1	1	1	

2) Implement following expression using NOR Gate only:

Truth Table With Proof:

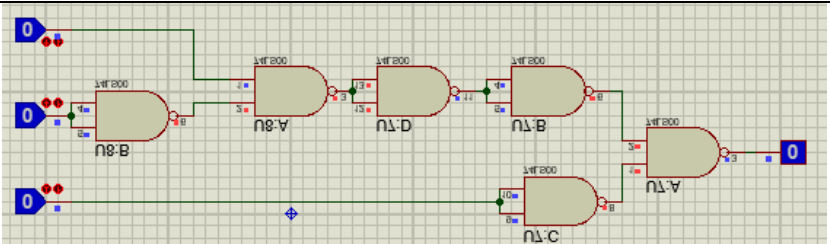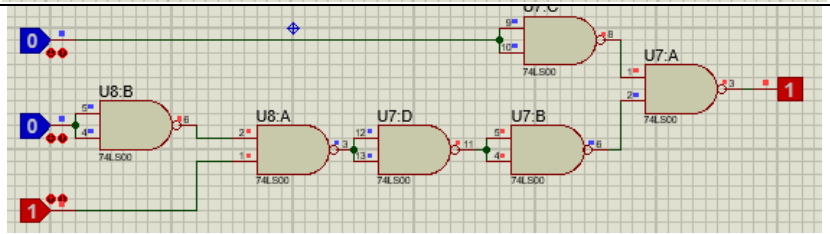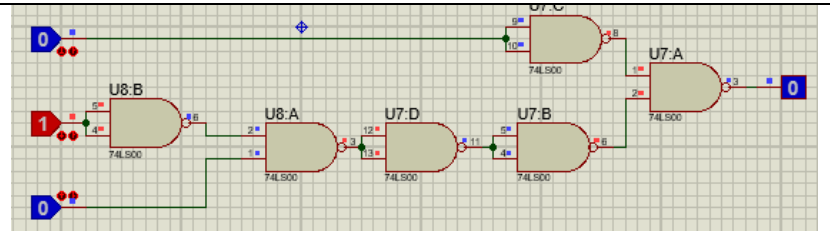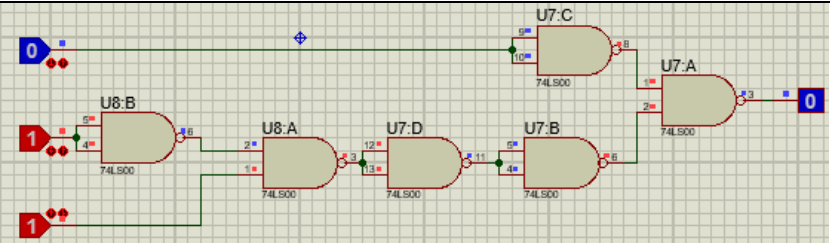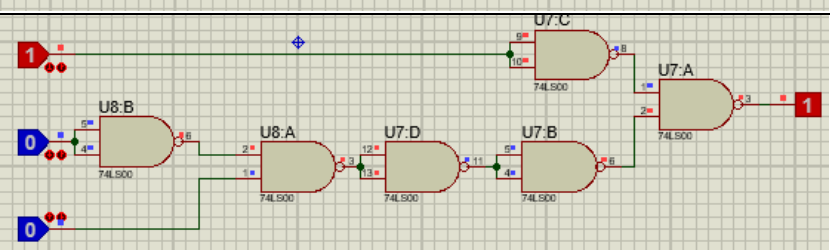Input			Output	Proof
X	Y	Z	F	
0	0	0	0	
0	0	1	1	
0	1	0	0	
0	1	1	0	
1	0	0	1	

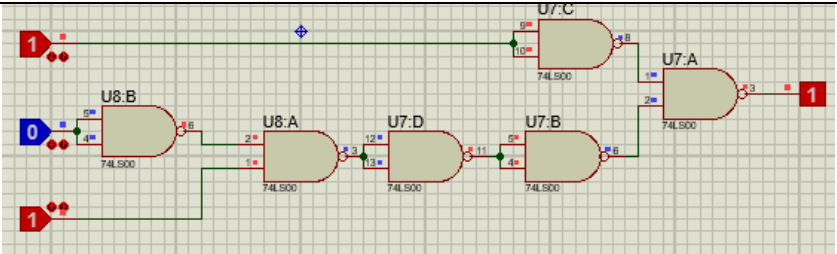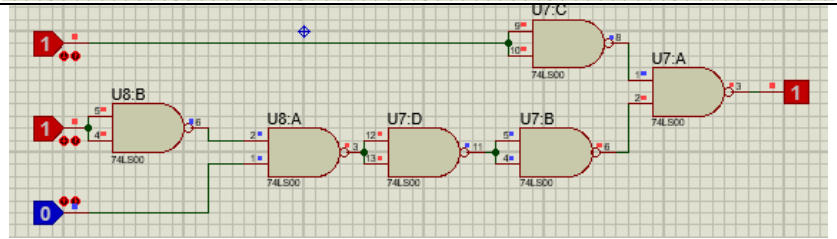1	0	1	1	
1	1	0	1	
1	1	1	1	