

Digital Logic Design (DLD)

(Lab Task No 4)



Session (2022-2026)

Program

BS-Computer Science

Submitted By:

Student Name: Shaheer Ali

Roll Number: 301221044

Supervised By:

Ms. Muneeba Darwaish

Lecturer

CS& IT Department

Hazara University, Mansehra

EXPERIMENT 04:

Implementation of a Half Adder and a Full Adder using gates.

Implementation of 4-bit Adder and Subtractor using 74LS83 & 74LS86.

Objectives:

To implement a half adder and a full adder using gates and implementing 4-bit adder and subtractor using 74LS83 & 74LS86.

Equipment/Tool:

Trainer, IC – XOR, IC-OR, IC-AND, IC74LS83 (4-bit adder), 74LS86 (XOR).

Background theory:

A half adder is a combinational circuit that adds two binary inputs. It gives two outputs, S as the sum and C as the carry of the inputs. A full adder is a combinational circuit that adds three binary inputs X, Y and Z. The input Z is the carry input from another addition. It gives two outputs, S as the sum and C as the carry of the inputs.

The circuit for the adder/subtractor shown in figure 4.3 is used to do binary additions and subtractions. If $C_{in}=0$, addition is performed and if $C_{in}=1$, subtraction is performed.

Tasks:

- Write a truth table for a half adder, design a simplified circuit for it. Implement it on trainer and verify the results.
- Write a truth table for a full adder, design a simplified circuit for it. Implement it on trainer and verify the results.
- Fill in the truth table.
- Design the complete circuit on the trainer and verify the results.

Procedure





Task 1 & 2

Fill in the following truth table of half adder and full adder and draw the circuit from

HALF ADDER

ANSWER:





Table for Half Adder:

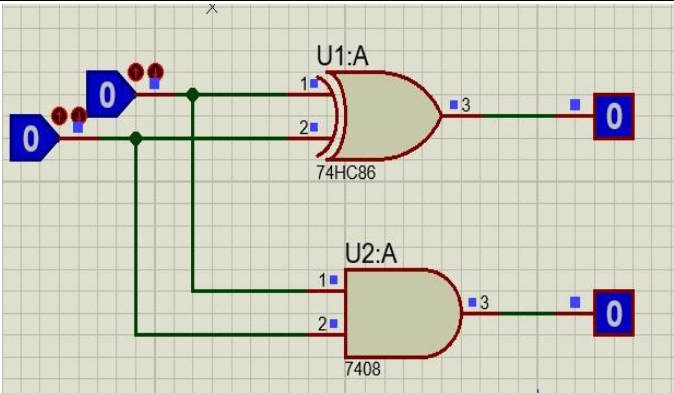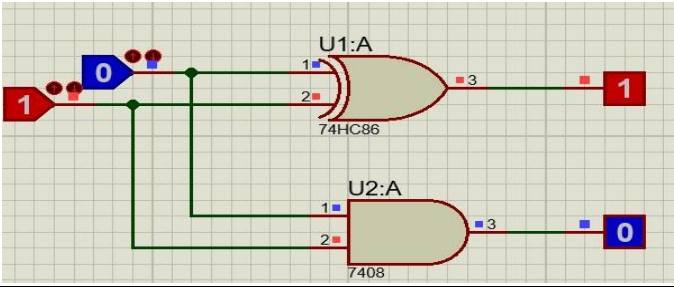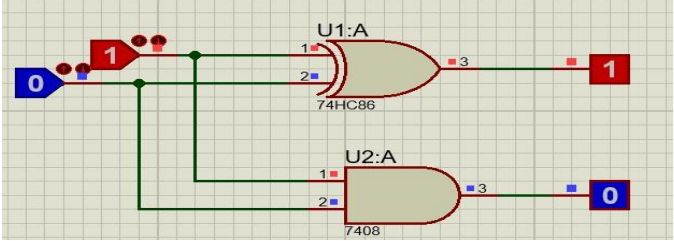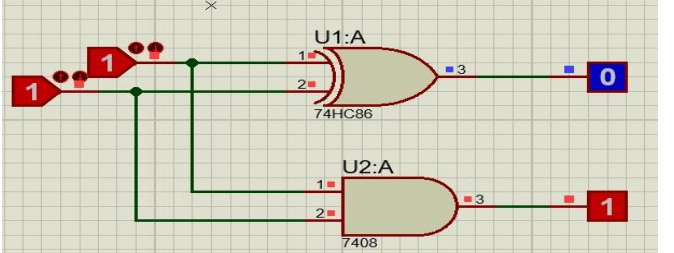A	B	Sum	Carry	Proof Circuits
0	0	0	0	
0	1	1	0	
1	0	1	0	
1	1	0	1	

FULL ADDER

ANSWER:

Table for Full Adder:

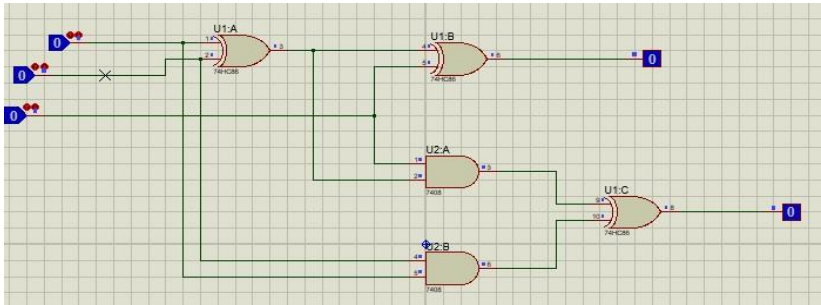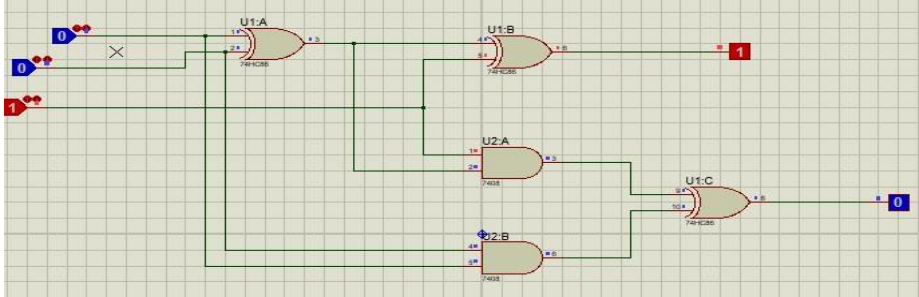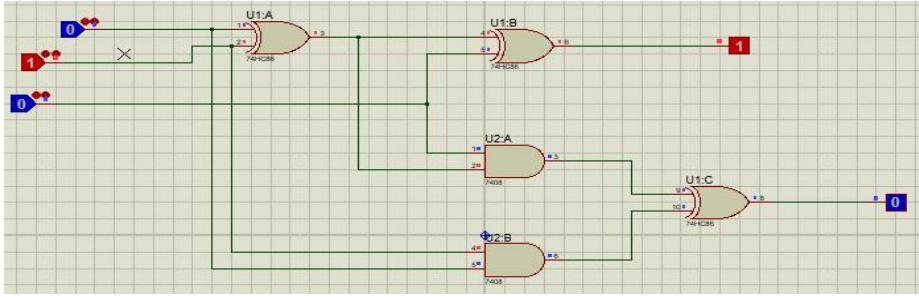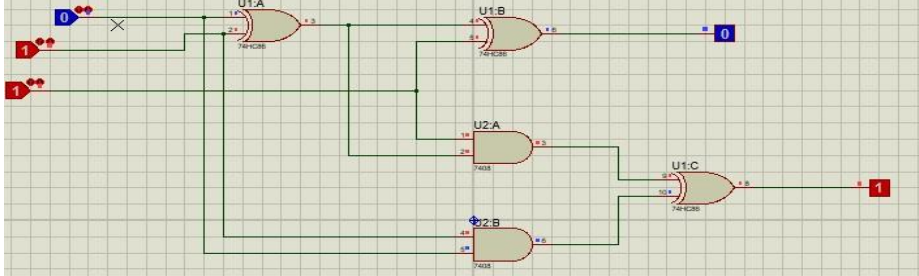A	B	C	Sum	Carry	Proof Circuits
0	0	0	0	0	
0	0	1	1	0	
0	1	0	1	0	
0	1	1	0	1	

1	0	0	1	0	
1	0	1	0	1	
1	1	0	0	1	
1	1	1	1	1	

Implementation of 4-bit Adder and Subtractor using 74LS83 & 74LS86.

Exercise in Lab:

Fill in the following truth table, verify your results, and show it to the instructor:-

A3	A2	A1	A0
B3	B2	B1	B0
S3	S2	S1	S0

Answer:

A3	A2	A1	A0
1	0	1	0
B3	B2	B1	B0
0	1	0	1
S3	S2	S1	S0
1	1	1	1

Verification:

