

DLD

Boolean Algebra, Operation and Expression


Department of Computer Science & IT

Hazara University Mansehra

Instructor: Muneeba Darwaish

Boolean Operations and Expressions

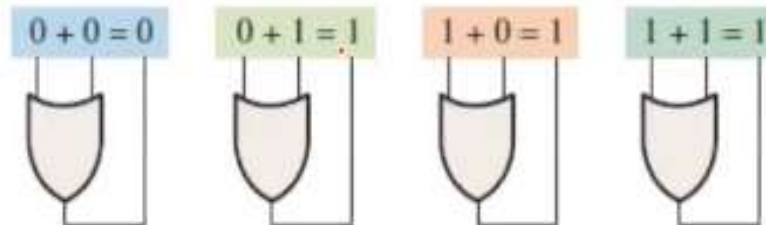
- Boolean algebra is the mathematics of digital logic.
- **Boolean Addition:** Boolean addition is equivalent to the OR operation.
- The basic rules are illustrated below:



- In logic circuits, a sum term is produced by an OR operation.
- Some examples of sum terms are $A + B$, $A + B + C$, and $A + B + C + D$.

Boolean Operations and Expressions

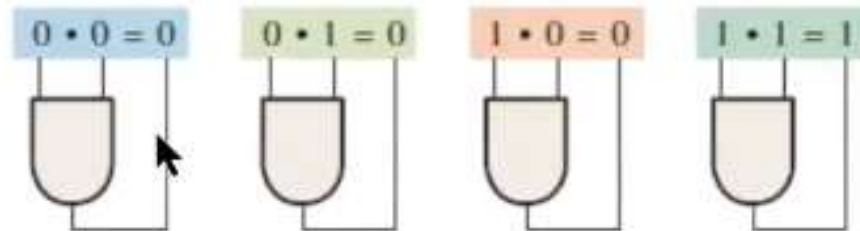- **Boolean multiplication** is equivalent to the AND operation.
- The basic rules are illustrated with their relation to the AND gate:



- Examples are: AB , $A\bar{B}$, ABC , and $A\bar{B}C\bar{D}$.
- A product term is equal to 1 only if each of the literals in the term is 1.
- A product term is equal to 0 when one or more of the literals are 0.

Boolean Operations and Expressions

- A sum term is equal to 1 when one or more of the literals in the term are 1.
- A sum term is equal to 0 only if each of the literals is 0.

EXAMPLE 4-1

Determine the values of A , B , C , and D that make the sum term $A + \overline{B} + C + \overline{D}$ equal to 0.

Solution

For the sum term to be 0, each of the literals in the term must be 0. Therefore, $A = 0$, $B = 1$ so that $\overline{B} = 0$, $C = 0$, and $D = 1$ so that $\overline{D} = 0$.

$$A + \overline{B} + C + \overline{D} = 0 + \overline{1} + 0 + \overline{1} = 0 + 0 + 0 + 0 = 0$$

EXAMPLE 4-2

Determine the values of A , B , C , and D that make the product term $A\bar{B}C\bar{D}$ equal to 1.

Solution

For the product term to be 1, each of the literals in the term must be 1. Therefore, $A = 1$, $B = 0$ so that $\bar{B} = 1$, $C = 1$, and $D = 0$ so that $\bar{D} = 1$.

$$A\bar{B}C\bar{D} = 1 \cdot \bar{0} \cdot 1 \cdot \bar{0} = 1 \cdot 1 \cdot 1 \cdot 1 = 1$$

Related Problem

Determine the values of A and B that make the product term $\bar{A}\bar{B}$ equal to 1.

DIY

1. If $A = 0$, what does \overline{A} equal?
2. Determine the values of A , B , and C that make the sum term $\overline{A} + \overline{B} + C$ equal to 0.
3. Determine the values of A , B , and C that make the product term $A\overline{B}C$ equal to 1.




Laws of Boolean Algebra

Commutative Laws

The *commutative law of addition* for two variables is written as

$$A + B = B + A$$

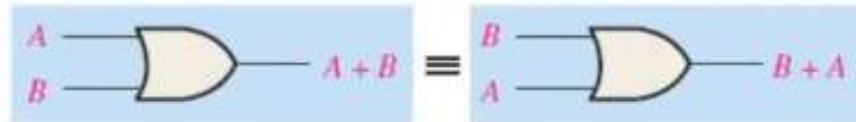

The *commutative law of multiplication* for two variables is

$$AB = BA$$




Laws of Boolean Algebra

Associative Laws

The *associative law of addition* is written as follows for three variables:

$$A + (B + C) = (A + B) + C$$

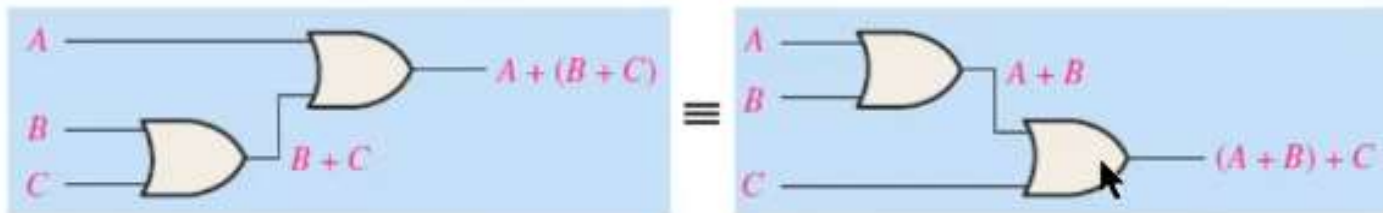


Laws of Boolean Algebra

Associative Laws


The *associative law of addition* is written as follows for three variables:

$$A + (B + C) = (A + B) + C$$

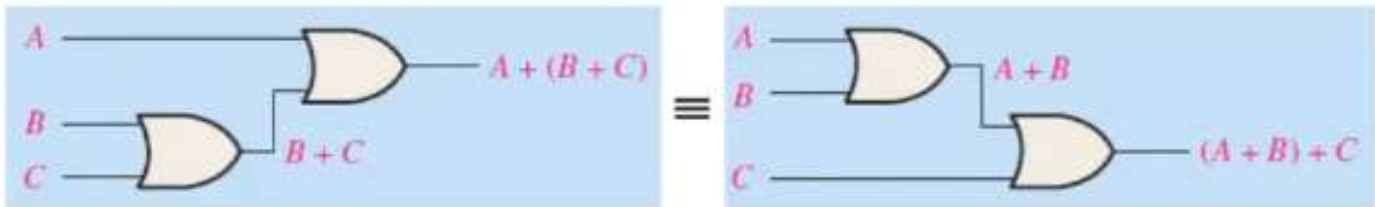

The *associative law of multiplication* is written as follows for three variables:

$$A(BC) = (AB)C$$

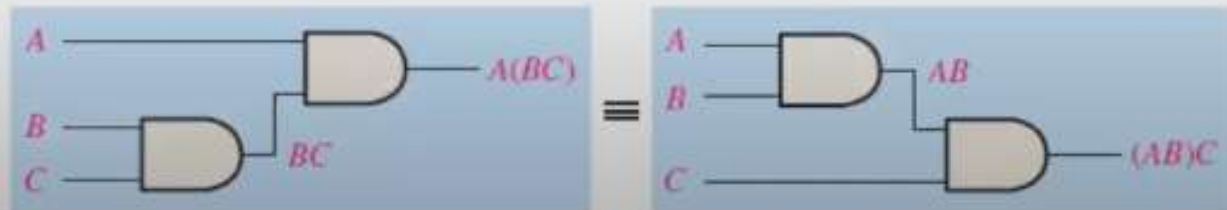


Laws of Boolean Algebra

Distributive Law

The distributive law is written for three variables as follows:

$$A(B + C) = AB + AC$$

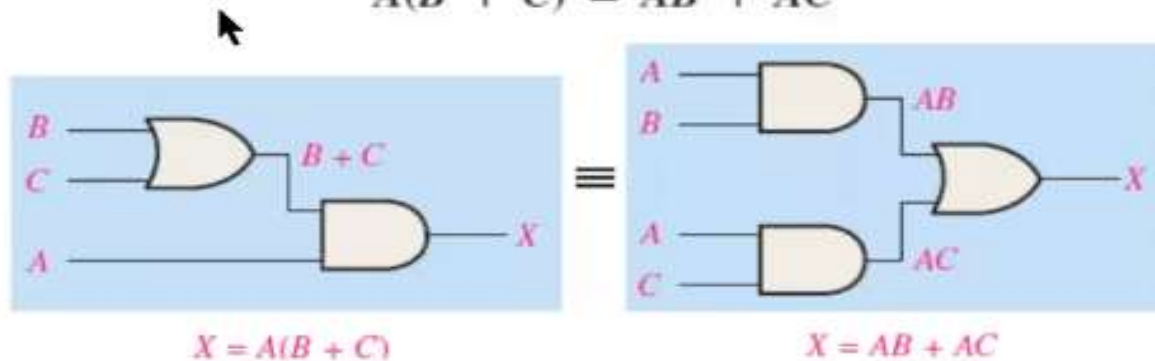

Rules of Boolean Algebra

Basic rules of Boolean algebra.

1. $A + 0 = A$

2. $A + 1 = 1$

3. $A \cdot 0 = 0$

4. $A \cdot 1 = A$

5. $A + A = A$

6. $A + \bar{A} = 1$

7. $A \cdot A = A$

8. $A \cdot \bar{A} = 0$

9. $\overline{\bar{A}} = A$


10. $A + AB = A$

11. $A + \bar{A}B = A + B$


12. $(A + B)(A + C) = A + BC$

Rules of Boolean Algebra

Rule 1. $A + 0 = A$

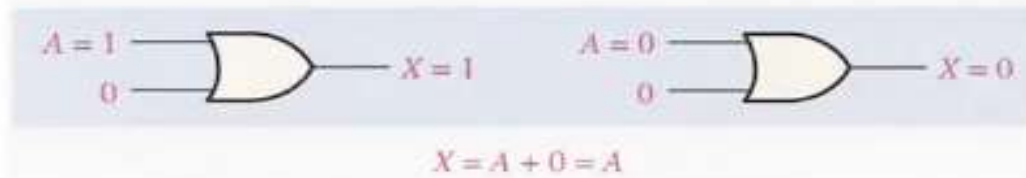


Rule 2. $A + 1 = 1$

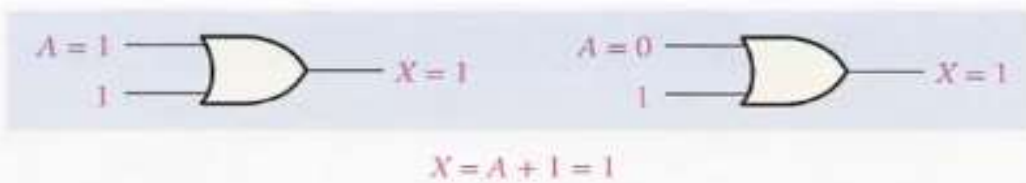


Rules of Boolean Algebra

Rule 3. $A \cdot 0 = 0$

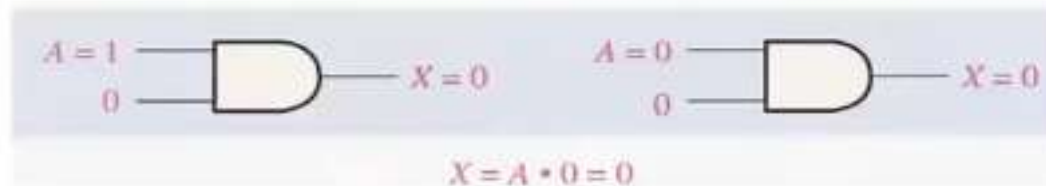


Rule 4. $A \cdot 1 = A$

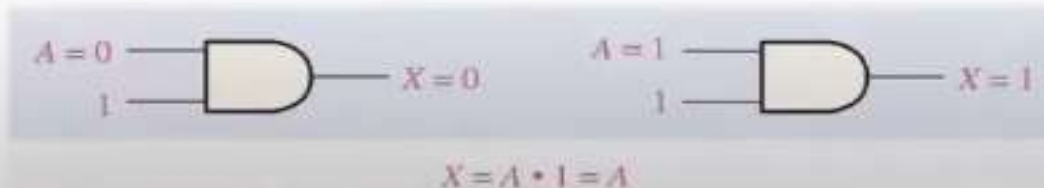


Rules of Boolean Algebra

Rule 5. $A + A = A$

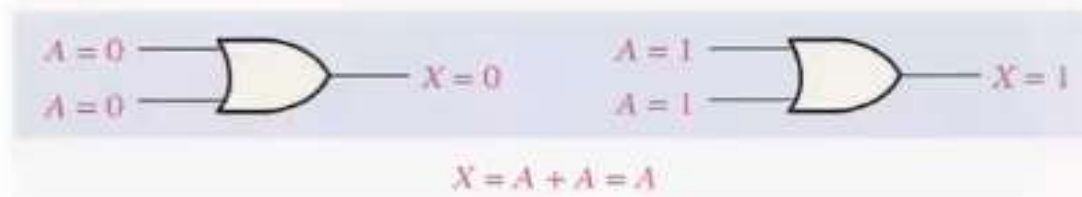


Rule 6. $A + \bar{A} = 1$

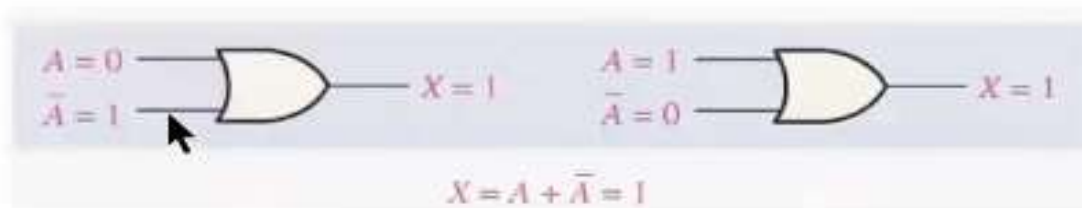


Rules of Boolean Algebra

Rule 7. $A \cdot A = A$

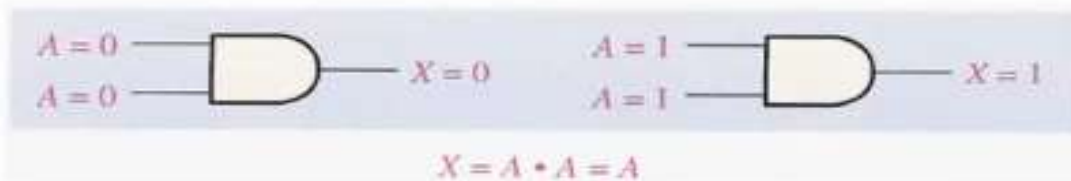

Rule 8. $A \cdot \bar{A} = 0$

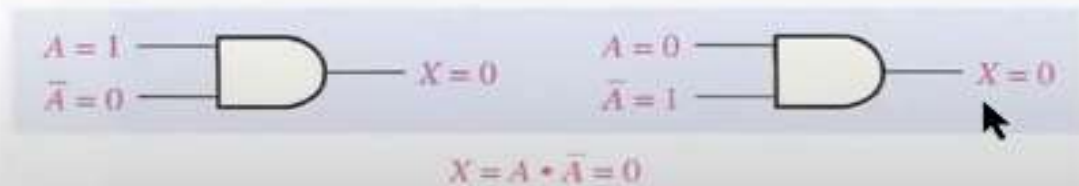

Rules of Boolean Algebra

Rule 9. $\overline{\overline{A}} = A$




Rules of Boolean Algebra

Rule 10. $A + AB = A$ This rule can be proved by applying the distributive law, rule 2, and rule 4 as follows:

$$\begin{aligned} A + AB &= A(1 + B) && \text{Factoring (distributive law)} \\ &= A \cdot 1 && \text{Rule 2: } (1 + B) = 1 \\ &= A && \text{Rule 4: } A \cdot 1 = A \end{aligned}$$

A	B	AB	A + AB
0	0	0	0
0	1	0	0
1	0	0	1
1	1	1	1

equal

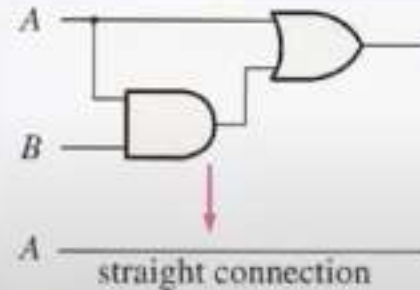

Rules of Boolean Algebra

Rule 11. $A + \bar{A}B = A + B$ This rule can be proved as follows:

$$\begin{aligned}
 A + \bar{A}B &= (A + AB) + \bar{A}B \\
 &= (AA + AB) + \bar{A}B \\
 &= AA + AB + A\bar{A} + \bar{A}B \\
 &= (A + \bar{A})(A + B) \\
 &= 1 \cdot (A + B) \\
 &= A + B
 \end{aligned}$$

Rule 10: $A = A + AB$

Rule 7: $A = AA$

Rule 8: adding $A\bar{A} = 0$


Factoring

Rule 6: $A + \bar{A} = 1$

Rule 4: drop the 1

A	B	$\bar{A}B$	$A + \bar{A}B$	$A + B$
0	0	0	0	0
0	1	1	1	1
1	0	0	1	1
1	1	0	1	1

↑ equal ↑

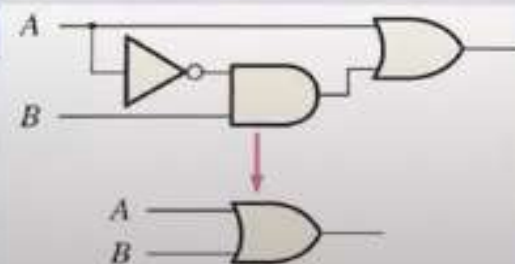


Rules of Boolean Algebra

Rule 12. $(A + B)(A + C) = A + BC$ This rule can be proved as follows:

$$\begin{aligned}
 (A + B)(A + C) &= AA + AC + AB + BC && \text{Distributive law} \\
 &= \underline{A} + AC + AB + BC && \text{Rule 7: } AA = A \\
 &= A(1 + C) + AB + BC && \text{Factoring (distributive law)} \\
 &= \underline{A \cdot 1} + AB + BC && \text{Rule 2: } \underline{1 + C = 1} \\
 &= \underline{A(1 + B)} + BC && \text{Factoring (distributive law)} \\
 &= \underline{A \cdot 1} + BC && \text{Rule 2: } 1 + B = 1 \\
 &= \underline{A + BC} && \text{Rule 4: } A \cdot 1 = A
 \end{aligned}$$

A	B	C	A + B	A + C	(A + B)(A + C)	BC	A + BC
0	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0
0	1	0	1	0	0	0	0
0	1	1	1	1	1	1	1
1	0	0	1	1	1	0	1
1	0	1	1	1	1	0	1
1	1	0	1	1	1	0	1
1	1	1	1	1	1	1	1

↑ equal ↑

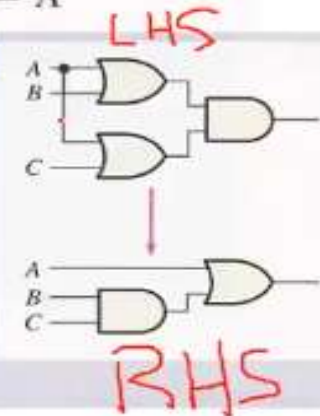

□

Expression Simplification

EXAMPLE 4-9

Using Boolean algebra techniques, simplify this expression:

$$AB + \underline{A(B + C)} + \underline{B(B + C)}$$

$$1. A + 0 = A$$

$$2. A + 1 = 1$$

$$3. A \cdot 0 = 0$$

$$4. A \cdot 1 = A$$

$$5. \underline{A + A = A}$$

$$6. \underline{A + \bar{A} = 1}$$

$$7. \underline{A \cdot A = A}$$

$$8. \underline{A \cdot \bar{A} = 0}$$

$$9. \bar{\bar{A}} = A$$

$$10. \underline{A + AB = A}$$

$$11. \underline{A + \bar{A}B = A + B}$$

$$12. (A + B)(A + C) = A + BC$$

A, B, or C can represent a single variable or a combination of variables.

Step 1: Apply the distributive law to the second and third terms in the expression, as follows:

$$AB + AB + AC + \underline{BB} + BC$$

Step 2: Apply rule 7 ($BB = B$) to the fourth term.

$$\underline{AB + AB} + AC + B + BC$$

Step 3: Apply rule 5 ($AB + AB = AB$) to the first two terms.

$$AB + AC + \underline{B + BC} \rightarrow B(1 + C)$$

Step 4: Apply rule 10 ($B + BC = B$) to the last two terms.

$$AB + AC + B$$

EXAMPLE 4-9

Using Boolean algebra techniques, simplify this expression:

$$AB + A(B + C) + B(B + C)$$

Step 4: Apply rule 10 ($B + BC = B$) to the last two terms.

$$\underline{AB} + AC + \underline{B}$$

1. $A + 0 = A$

2. $A + 1 = 1$

3. $A \cdot 0 = 0$

4. $A \cdot 1 = A$

5. $A + A = A$

6. $A + \bar{A} = 1$

7. $A \cdot A = A$

8. $A \cdot \bar{A} = 0$

9. $\bar{\bar{A}} = A$

10. $A + AB = A$

11. $A + \bar{A}B = A + B$

12. $(A + B)(A + C) = A + BC$

A, B, or C can represent a single variable or a combination of variables.

$$B + AB$$

Step 5: Apply rule 10 ($AB + B = B$) to the first and third terms.

$$\underline{B} + AC$$

At this point the expression is simplified as much as possible. Once you gain experience in applying Boolean algebra, you can often combine many individual steps.

EXAMPLE 4-9

Using Boolean algebra techniques, simplify this expression:

$$AB + A(B + C) + B(B + C)$$

Step 4: Apply rule 10 ($B + BC = B$) to the last two terms.

$$\underline{AB} + AC + \underline{B}$$

$$1. A + 0 = A$$

$$2. A + 1 = 1$$

$$3. A \cdot 0 = 0$$

$$4. A \cdot 1 = A$$

$$5. A + A = A$$

$$6. A + \bar{A} = 1$$

$$7. A \cdot A = A$$

$$8. A \cdot \bar{A} = 0$$

$$9. \bar{\bar{A}} = A$$

$$10. A + AB = A$$

$$11. A + \bar{A}B = A + B$$

$$12. (A + B)(A + C) = A + BC$$

A , B , or C can represent a single variable or a combination of variables.

$$B + AB$$

Step 5: Apply rule 10 ($AB + B = B$) to the first and third terms.

$$\underline{B} + AC$$

At this point the expression is simplified as much as possible. Once you gain experience in applying Boolean algebra, you can often combine many individual steps.

