


Digital Logic & Design

Hazara University Mansehra
Department of Computer Science & IT

Introduction


- Now we discuss some of the major functions of Combinational Logic including:
 - Adders,
 - Comparators,
 - Decoders,
 - Encoders,
 - Code Converters,
 - Multiplexers (data selectors),
 - Demultiplexers, and
 - Parity generators/checkers
- 

Half and Full Adders

- Adders are important in computers and also in other types of digital systems in which numerical data are processed.
- An understanding of the basic adder operation is fundamental to the study of digital systems.
- In this section, the half-adder and the full-adder are introduced.

The Half-Adder

 - A half-adder adds two bits and produces a sum and an output carry.



$$\begin{array}{r} 1 \\ 1 \\ \hline 10 \end{array}$$

TABLE 6-1

Half-adder truth table

<i>A</i>	<i>B</i>	<i>C_{out}</i>	<i>Σ</i>
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Σ = sum


C_{out} = output carry

A and *B* = input variables (operands)

$$\begin{array}{l} 0 + 0 = 0 \\ 0 + 1 = 1 \\ 1 + 0 = 1 \\ 1 + 1 = 10 \end{array}$$

The Half-Adder

 - A half-adder adds two bits and produces a sum and an output carry.



$$\begin{array}{r} 1 \\ 1 \\ \hline 10 \\ C = 1 \end{array}$$

TABLE 6-1

Half-adder truth table

A	B	C_{out}	Σ
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$\begin{array}{l} 0 + 0 = 0 \\ 0 + 1 = 1 \\ 1 + 0 = 1 \\ 1 + 1 = 10 \end{array}$$

Σ = sum

C_{out} = output carry

A and B = input variables (operands)

$$\Sigma = \bar{A}B + A\bar{B}$$

$$C_{out} = A \oplus B$$

$$C_{out} = AB$$

The Half-Adder


- From the operation of the half-adder as stated in Table 6–1, expressions can be derived for the sum and the output carry as functions of the inputs.
- Notice that the output carry (C_{out}) is a 1 only when both A and B are 1s; therefore, C_{out} can be expressed as the AND of the input variables.

$$C_{out} = AB$$

- Now observe that the sum output is a 1 only if the input variables, A and B , are not equal.
- The sum can therefore be expressed as the exclusive-OR of the input variables.


$$\Sigma = A \oplus B$$

Half-Adder Logic Diagram

 

The Full-Adder

 - The second category of adder is the full-adder.
- The full-adder accepts two input bits and an input carry and generates a sum output and an output carry.



$$\Sigma = (A \oplus B) \oplus C_{in}$$

$$C_{out} = AB + (A \oplus B)C_{in}$$

TABLE 6-2

Full-adder truth table.

A	B	C_{in}	C_{out}	Σ
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

C_{in} = input carry, sometimes designated as CI

C_{out} = output carry, sometimes designated as CO


Engr.Hammur Σ = sum

A and B = input variables (operands)

Full-Adder Logic Diagram




 (a) Logic required to form the sum of three bits




(b) Complete logic circuit for a full-adder (each half-adder is enclosed by a shaded area)

Arrangement of two half-adders to form a full-adder

 


 EXAMPLE 6-1


For each of the three full-adders in Figure 6-6, determine the outputs for the inputs shown.



(a)

 

(b)

 

(c)


SECTION 6-1 CHECKUP

Answers are at the end of the chapter.

- Determine the sum (Σ) and the output carry (C_{out}) of a half-adder for each set of input bits:
(a) 01 (b) 00 (c) 10 (d) 11
- A full-adder has $C_{in} = 1$. What are the sum (Σ) and the output carry (C_{out}) when $A = 1$ and $B = 1$?

Parallel Binary Adders

 - A single full-adder is capable of adding two 1-bit numbers and an input carry.
- To add binary numbers with more than one bit, you must use additional full-adders. When one binary number is added to another, each column generates a sum bit and a 1 or 0 carry bit to the next column to the left, as illustrated here with 2-bit numbers.




$$\begin{array}{r}
 C_0 \\
 11 \\
 01 \\
 \hline
 100 \\
 C_2, \Sigma_2, \Sigma_1
 \end{array}$$

Parallel Binary Adders

- To add two binary numbers, a full-adder (FA) is required for each bit in the numbers.
- So for 2-bit numbers, two adders are needed; for 4-bit numbers, four adders are used; and so on.
- The carry output of each adder is connected to the carry input of the next higher-order adder

General format, addition
of two 2-bit numbers:

 
$$\begin{array}{r} A_2 A_1 \\ + B_2 B_1 \\ \hline \Sigma_3 \Sigma_2 \Sigma_1 \end{array}$$





Parallel Binary Adders

 EXAMPLE 6-2

Determine the sum generated by the 3-bit parallel adder in Figure 6-8 and show the intermediate carries when the binary numbers 101 and 011 are being added.



  

Truth table for each stage of a 4-bit parallel adder.


C_{x-1}	A_x	B_x	Σ_x	C_x
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Four-Bit Parallel Adders

- A group of four bits is called a **Nibble**.
- A basic 4-bit parallel adder is implemented with four full-adder stages as shown in Figure,
- Again, the LSBs (A1 and B1) in each number being added go into the right-most full-adder; the higher-order bits are applied as shown to the successively higher-order adders, with the MSBs (A4 and B4) in each number being applied to the left-most full-adder.
- The carry output of each adder is connected to the carry input of the next higher-order adder as indicated.
- These are called internal carries.

Adder Expansion

 - The 4-bit parallel adder can be expanded to handle the addition of two 8-bit numbers by using two 4-bit adders.
- The carry input of the low-order adder (C_0) is connected to ground because there is no carry into the least significant bit position, and the carry output of the low-order adder is connected to the carry input of the high-order adder, as shown in Figure:



Application

An example of full-adder and parallel adder application is a simple voting system that can be used to simultaneously provide the number of “yes” votes and the number of “no” votes. This type of system can be used where a group of people are assembled and there is a need for immediately determining opinions (for or against), making decisions, or voting on certain issues or other matters.

In its simplest form, the system includes a switch for “yes” or “no” selection at each position in the assembly and a digital display for the number of yes votes and one for the number of no votes. The basic system is shown in Figure 6–13 for a 6-position setup, but it can be expanded to any number of positions with additional 6-position modules and additional parallel adder and display circuits.

